

Neuromorphic engineering I

## Lab 5: Static Circuits: Transconductance Amplifier

Team member 1: Quillan Favey

Group number:

Date: 10.25.22

---

### Lab objectives

The objectives of this lab are to understand and characterize one of the most important circuit in analog IC design.

The experimental objectives are as follows:

1. To characterize a simple differential transconductance amplifier and understand its operation in terms of the behavior of the differential pair and the current mirror. Specifically, to understand the dependence of the output current on the differential input voltages.
2. To characterize single-stage 2-transistor "common-source" amplifier gain, and how it arises from transconductance and output impedance.

## 1 Prelab

### 1.1 Transconductance amplifier

- Now consider a simple differential transconductance amplifier which is built from a differential pair and a current mirror. The output current should be equal to the the difference of the two differential pair currents, i. e.  $I_{out} = I_1 - I_2$ . Is this statement true? Justify your answer by stating your assumptions about transistor saturation and drain conductance.

Yes, as long as all MOSFETs are in saturation ( $V_s > 4U_T$ ) and the diff. pair is operated below threshold. This restricts our output voltage range to:

$$V_s + 4U_T < V_{OUT} < V_{dd} - 4U_T \quad (1)$$

If we have a look at the case where  $V_1 = V_2$ , the current flowing through each branch will be  $\frac{I_b}{2}$

The drain conductance ( $g_{md} = \frac{-\delta I_{out}}{\delta V_{out}}$ ) in these conditions (saturation, subthreshold and

assuming  $V_E$  is the same for every MOSFET) can be written as:

$$g_{md} = g_{ds} = \frac{I_4}{V_E} + \frac{I_2}{V_E} \quad (2)$$

$$g_{ds} = \frac{I_b}{2V_E} + \frac{I_b}{2V_E} \quad (3)$$

$$g_{ds} = \frac{I_b}{V_E} \quad (4)$$

Where  $V_E$  is the early voltage.

Also by applying KCL we can verify this statement .

- Now consider the transconductance amplifier with the output open-circuited (i.e. no current flows into or out of the output node). Say  $V_2$  is fixed at some voltage in the middle of the rails, e.g.,  $\frac{V_{dd}}{2}$ . Explain what happens to the output voltage as  $V_1$  is swept from below  $V_2$  to above  $V_2$  for a subthreshold bias. Discuss the current through the differential pair transistors and the current mirror, and the voltage on the internal node common to the differential pair transistors. Try to keep the discussion concise.

The equation for  $V_{out}$  in a transconductance amplifier is the following:

$$V_{out} = A(V_1 - V_2) \quad (5)$$

In subthreshold,

$$A \approx \frac{\kappa V_E}{2U_T} \quad (6)$$

- For  $V_1 < V_2$ :

$I_2$  is equal to  $I_b$  and  $I_1$  is 0, therefore the current in the current mirror is also 0. Which will lead to a discharge in the "node capacitor" and the M2 NFET voltage will drop to 0 and as M2 goes out of saturation,  $V_{out} \approx V_s$ .

- For  $V_1 > V_2$ :

$I_1$  is equal to  $I_b$  and  $I_2$  is 0, therefore the current in the mirror is  $I_b$  which will lead to charging of the "node capacitor" and eventually M5 will go out of saturation as  $V_{out}$  will go up to Vdd.

- What is the transconductance  $g_m = \frac{dI_{out}}{dV_{in}}$ , where  $V_{in} \equiv V_1 - V_2$ , in sub-threshold? How does it change if the circuit is operated super-threshold?

In sub-threshold:  $g_m = \frac{I_b \kappa}{2U_T}$

In super-threshold:  $g_m = \sqrt{\beta I_b}$  for  $|V_1 - V_2| < \sqrt{2I_b/\beta}$

- Quantitatively, what is the relationship between transconductance, output resistance  $r_o$ , and voltage gain  $A$  of a transconductance amplifier?


$$gd = \frac{Ib}{V_E} \quad (7)$$

$$r_o = \frac{1}{g_d} = \frac{V_E}{I_b} \quad (8)$$

$$A = \frac{dV_{out}}{d(v_1 - V_2)} = \frac{dI_{out}}{d(v_1 - V_2)} \frac{dV_{out}}{dI_{out}} = \frac{g_m}{g_d} = g_m r_o = \frac{I_b \kappa}{2U_T} r_o \quad (9)$$
 
## 1.2 Wide-Range Transamp

- Draw the schematic of a wide-range transconductance amplifier and explain why it does not have the simple 5-transistor transamp restriction on allowable output voltage. You can either draw the schematic directly on the Jupyter notebook using the *schemdraw*, or sketch it with pen and paper and paste a picture in a Markdown cell.



The current mirror transistors, in order to be in saturation need a  $V_g$  that is lower than  $V_{dd} - 4U_T$  so  $V_s$  must satisfy this condition as well.  $V_s$  must also keep M3 in saturation and must therefore be greater than  $4U_T$ . We end up with  $I_1$  charging the "capacitor node" at  $I_{out}$  and  $I_2$  discharging it. And the only boundary on  $V_{out}$  is then  $4U_T$

## 2 Setup

### 2.1 Connect the device

```
In [ ]: # import the necessary library to communicate with the hardware
import pyplane

import time
import numpy as np
import matplotlib.pyplot as plt
```

```
In [ ]: # create a Plane object and open the communication
if 'p' not in locals():
    p = pyplane.Plane()
    try:
        p.open('/dev/ttyACM0')
    except RuntimeError as e:
        del p
        print(e)
```

```
In [ ]: p.get_firmware_version()
```

```
Out[ ]: (1, 8, 4)
```

```
In [ ]: # Send a reset signal to the board, check if the LED blinks
p.reset(pyplane.ResetType.Soft)

time.sleep(0.5)
# NOTE: You must send this request events every time you do a reset operation, otherwise
# Because the class chip need to do handshake to get the communication correct.
p.request_events(1)
```

```
In [ ]: # Try to read something, make sure the chip responses
p.read_current(pyplane.AdcChannel.G00_N)
```

```
Out[ ]: 1.7724609335800778e-07
```

```
In [ ]: # If any of the above steps fail, delete the object, and restart the kernel
# del p
```

### 2.2 Setup C2F and voltage output buffer

```
In [ ]: # setup C2F
p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
    pyplane.Coach.BiasAddress.C2F_HYS_P, \
    pyplane.Coach.BiasType.P, \
    pyplane.Coach.BiasGenMasterCurrent.I60pA, 100)])

time.sleep(0.2)
p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
    pyplane.Coach.BiasAddress.C2F_BIAS_P, \
    pyplane.Coach.BiasType.P, \
```

```

pyplane.Coach.BiasGenMasterCurrent.I240nA, 255)])

time.sleep(0.2)
p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
    pyplane.Coach.BiasAddress.C2F_PWLK_P, \
    pyplane.Coach.BiasType.P, \
    pyplane.Coach.BiasGenMasterCurrent.I240nA, 255)])

time.sleep(0.2)
p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
    pyplane.Coach.BiasAddress.C2F_REF_L, \
    pyplane.Coach.BiasType.N, \
    pyplane.Coach.BiasGenMasterCurrent.I30nA, 255)])


time.sleep(0.2)
p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
    pyplane.Coach.BiasAddress.C2F_REF_H, \
    pyplane.Coach.BiasType.P, \
    pyplane.Coach.BiasGenMasterCurrent.I30nA, 255)])

time.sleep(0.2)
# setup output rail-to-rail buffer
p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
    pyplane.Coach.BiasAddress.RR_BIAS_P, \
    pyplane.Coach.BiasType.P, \
    pyplane.Coach.BiasGenMasterCurrent.I240nA, 255)])

```

## 3 N-Type 5T Transamp

### 3.0 Schematic and pin map

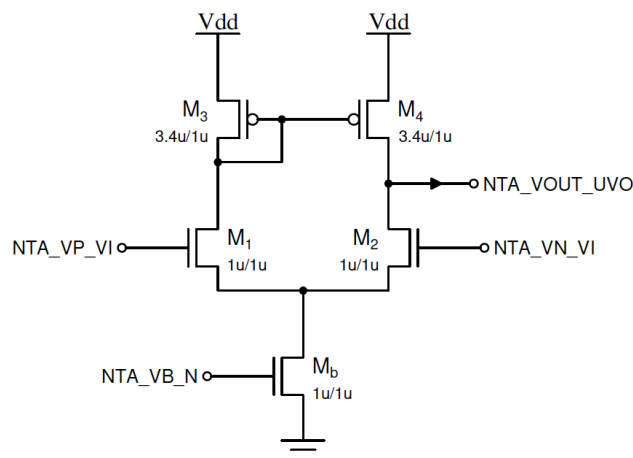

$$V_1 = V_p = \text{NTA\_VP\_VI} = \text{AIN3}$$

$$V_2 = V_n = \text{NTA\_VN\_VI} = \text{AIN4}$$

$$V_{out} = \text{NTA\_VOUT\_UVO} = \text{ADC}[13]$$

$$I_{out} = I_+ - I_- = \text{NTA\_IOUT\_UO} - \text{NTA\_IOUT\_UBO} = \text{C2F}[11] - \text{C2F}[12]; \text{ Note that } I_+ \text{ and } I_- \text{ is not } I_1 \text{ and } I_2.$$

**Note:** There are three identical NTA circuits with the same bias and input voltages, one with the output open-circuited and routed out at NTA\_VOUTUVO, the other two with  $V_{out}$  fixed to 1V but  $I_{out}$  routed out through N- and P- type current mirror at NTA\_IOUT\_UO and NTA\_IOUT\_UBO.

## 3.1 Chip configuration

```
In [ ]: # configure N type TransAmp
p.send_coach_events([pyplane.Coach.generate_aerc_event( \
    pyplane.Coach.CurrentOutputSelect.SelectLine5, \
    pyplane.Coach.VoltageOutputSelect.SelectLine1, \
    pyplane.Coach.VoltageInputSelect.SelectLine2, \
    pyplane.Coach.SynapseSelect.NoneSelected, 0)])
```

## 3.2 Calibration of C2F channels

Here you need to calibrate NTA\_IOUT\_UO and NTA\_IOUT\_UBO in the same way as the last lab

### 3.2.1 NTA\_IOUT\_UO

- Set fixed voltages for  $V_1$  and  $V_2$

```
In [ ]: p.set_voltage(pyplane.DacChannel.AIN3,0.8) # V1 = 0.8
time.sleep(0.2) # settle time
p.set_voltage(pyplane.DacChannel.AIN4,0.2) # V2 = 0.2
```

```
Out[ ]: 0.19882699847221375
```

Set voltages such that  $V_1 \gg V_2$ .

- Data acquisition (Hint: use master current for  $I_b = 30$  nA)

```
In [ ]: import numpy as np
import time

calIout_UO_ex3 = np.arange(0,85,1) # bias current sweep range, fine value
c2f_Iout_UO_ex3 = [] # what you get is frequency

for n in range(len(calIout_UO_ex3)):

    # set bias
    p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
        pyplane.Coach.BiasAddress.NTA_VB_N, \
        pyplane.Coach.BiasType.N, \
        pyplane.Coach.BiasGenMasterCurrent.I30nA, calIout_UO_ex3[n])])

    time.sleep(0.2) # settle time
```


```
# read c2f values
c2f_Iout_U0_ex3_temp = p.read_c2f_output(0.1)
c2f_Iout_U0_ex3.append(c2f_Iout_U0_ex3_temp[11])

print(c2f_Iout_U0_ex3)
```

```
[2, 89, 167, 251, 325, 409, 487, 568, 627, 709, 786, 867, 943, 1022, 1097, 1180, 1220, 1305, 1377, 1457, 1530, 1613, 1687, 1767, 1825, 1907, 1982, 2064, 2135, 2215, 2290, 2371, 2328, 2420, 2497, 2567, 2640, 2718, 2791, 2874, 2929, 3015, 3093, 3187, 3242, 3336, 3403, 3484, 3523, 3611, 3685, 3766, 3832, 3904, 3980, 4058, 4111, 4188, 4265, 4344, 4412, 4487, 4565, 4639, 4259, 4338, 4413, 4494, 4561, 4635, 4710, 4815, 4870, 4948, 4996, 5103, 5150, 5225, 5297, 5379, 5442, 5517, 5571, 5651, 5715]
```

- Plot
 
```
In [ ]: plt.plot(c2f_Iout_U0_ex3, '.k')
plt.show()
```



- Save data

```
In [ ]: # if the data looks nice, save it!
data_Iout_U0_ex3_cal= [c2f_Iout_U0_ex3, calIout_U0_ex3]
# save to csv file
np.savetxt('./data/c2f_Iout_U0_ex3_cal.csv', data_Iout_U0_ex3_cal, delimiter=',')
```

- Load data you saved

```
In [ ]: # Load the saved data
c2f_Iout_U0_ex3_save, calIout_U0_ex3_save = np.loadtxt('./data/c2f_Iout_U0_ex3_cal.csv',
```

- C2f plot

```
In [ ]: # C2f plot
import matplotlib.pyplot as plt
import numpy as np
plt.rcParams.update({'font.size': 14})
```

```

Iout_U0_ex3 = calIout_U0_ex3_save/256*30

plt.plot(Iout_U0_ex3,c2f_Iout_U0_ex3_save,'k+')

plt.xlabel('$I_b$ (nA)')
plt.ylabel('C2F (Hz)')
# plt.legend(['C2F'],prop={'size': 14})
plt.title('Fig. 1: C2F values vs. $I_{1}$ for $V_1 \gg V_2$.')
plt.grid()
plt.show()

```

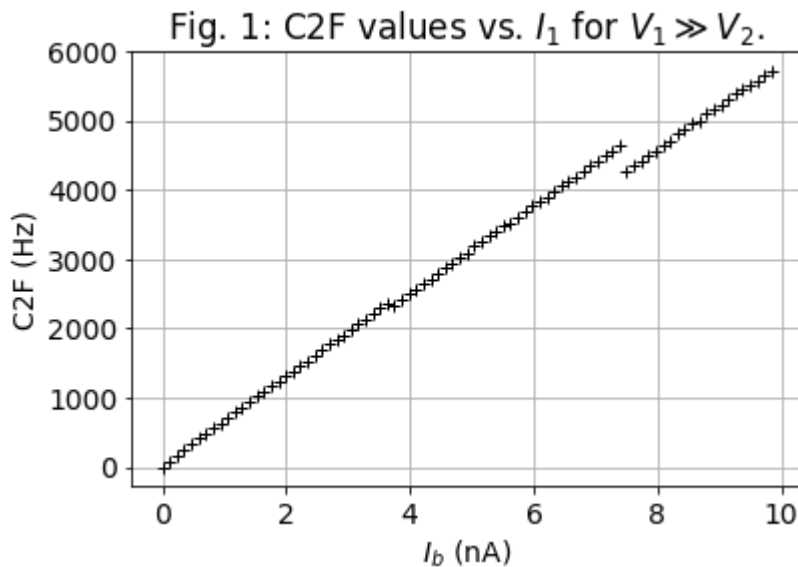


Fig. 1 shows the C2F values obtained by sweeping the bias current over the range  $I_b \in [0\text{nA}, 10\text{nA}]$ , whereas  $V_1 = 0.8\text{V}$  and  $V_2 = 0.2\text{V}$ .

The values for  $V_1$  and  $V_2$  were chosen such that  $V_1 \gg V_2$ . For these values, the corresponding currents becomes  $I_1 \approx I_b$  and  $I_2 \approx 0$ . The measured data can therefore be utilized to determine the mapping between  $I_1 \approx I_b$  and the C2F measurements for the transconductance amplifier.

- Extract the function  $I_+(f_+)$  (Hint: use higher order polynomial to increase accuracy)

```

In [ ]: # plot the raw data
raw_U0, = plt.plot(c2f_Iout_U0_ex3_save, Iout_U0_ex3, '.k')

# data range you want to fit
low_bound = 2
high_bound = 80
# print(c2f_Iout_U0_ex3[low_bound:high_bound])

# fit polynomial to C2F (frequency) vs I data
a2, a1, a0 = np.polyfit(c2f_Iout_U0_ex3_save[low_bound:high_bound], Iout_U0_ex3[low_bound:high_bound], 2)
# print(a0)
# print(a1)
# print(a2)

# Print out the function I(f) you got
I_freq = np.polyfit(c2f_Iout_U0_ex3_save[low_bound:high_bound], Iout_U0_ex3[low_bound:high_bound], 2)

```



```

print ('The I1(f1) function of NTA_IOUT_U0 is :')
print (np.poly1d(I_freq))

# select frequency range that you want to plot
freq = np.arange(0, 6000, 50)
# print(freq)

I1 = a2*freq**2 + a1*freq + a0 # function I(f),
fit, = plt.plot(freq, I1, 'r-', linewidth=2)


plt.xlabel('$f_1$ (Hz)', {'size':20})
plt.ylabel('$I_1$ (nA)', {'size':20})
plt.legend([fit, raw_U0], ['$I_1(f_1)$', 'raw data'],prop={'size': 14})
plt.title('Fig. 2: $I_1$ plotted as a function of $f_1$. ')
plt.grid()
plt.show()

```

The  $I_1(f_1)$  function of NTA\_IOUT\_U0 is :

$$6.842e-08 x^2 + 0.00135 x + 0.07457$$

Fig. 2:  $I_1$  plotted as a function of  $f_1$ .

 

### 3.2.2 NTA\_IOUT\_UBO

- Set fixed voltages for  $V_1$  and  $V_2$

```

In [ ]: p.set_voltage(pyplane.DacChannel.AIN3,0.2) # V1 = 0.8
time.sleep(0.2) # settle time
p.set_voltage(pyplane.DacChannel.AIN4,0.8) # V2 = 0.2

```

Set voltages such that  $V_1 \ll V_2$ .

- Data acquisition (Hint: use master current for  $I_b$  30 nA)

```

In [ ]: import numpy as np
import time

```

```
calIout_UBO_ex3 = np.arange(0,85,1) # bias current sweep range

c2f_Iout_UBO_ex3 = []

for n in range(len(calIout_UBO_ex3)):

    # set bias
    p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
pyplane.Coach.BiasAddress.NTA_VB_N, \
pyplane.Coach.BiasType.N, \
pyplane.Coach.BiasGenMasterCurrent.I30nA, calIout_UBO_ex3[n])])

    time.sleep(0.2) # settle time

    # read c2f values
    c2f_Iout_UBO_ex3_temp = p.read_c2f_output(0.1)
    c2f_Iout_UBO_ex3.append(c2f_Iout_UBO_ex3_temp[12])

print(c2f_Iout_UBO_ex3)
```

- Plot

```
In [ ]: plt.plot(c2f_Iout_UBO_ex3, '.k')
plt.show()
```

- Save data

```
In [ ]: # if the data looks nice, save it!
```

- Load data you saved

```
In [ ]:
```

- Extract the function  $I_-(f_-)$  (Hint: use second-order polynomial to increase accuracy)

```
In [ ]:
```

## 3.3 Output voltage vs. input voltage

### 3.3.1 Basic measurement

- Set bias current  $I_b$

```
In [ ]: p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
pyplane.Coach.BiasAddress.NTA_VB_N, \
pyplane.Coach.BiasType.N, \
pyplane.Coach.BiasGenMasterCurrent.I30nA, ???)])
```

The bias current is set to

$$I_b = w \frac{BG_{\text{fine}}}{256} I_{BG_{\text{master}}} = \frac{???}{256} \cdot 30\text{nA} \approx ???\text{nA}.$$

- Set fixed value of  $V_2$  (Hint: use `get_set_voltage` to get the real value set on the DAC)

```
In [ ]: p.set_voltage(pyplane.DacChannel.AIN4, ...) # V2 = ?
v2_real = p.get_set_voltage(pyplane.DacChannel.AIN4)
print("V2 is set to {} V".format(v2_real))
```

- Sweep  $V_1$  and measure  $V_{out}$  (Hint: use `get_set_voltage` to get the real value set on the DAC)

```
In [ ]: import numpy as np
import time

V1_sweep_ex3 = np.arange(0,1.8,0.05) # voltage V1 sweep range

V2_ex3_getset = p.get_set_voltage(pyplane.DacChannel.AIN4)

Vout_V1_sweep_ex3 = []
V1_sweep_ex3_getset = []

for n in range(len(V1_sweep_ex3)):

    p.set_voltage(pyplane.DacChannel.AIN3,V1_sweep_ex3[n]) #

    time.sleep(0.3) # settle time

    V1_sweep_ex3_getset.append(p.get_set_voltage(pyplane.DacChannel.AIN3))
    # Vout_V1_sweep_ex3.append(p.read_adc_instantaneous(13))
    Vout_V1_sweep_ex3.append(p.read_voltage(pyplane.AdcChannel.AOUT13))

# print(V2_ex3_getset)
# print(V1_sweep_ex3_getset)
# print(Vout_V1_sweep_ex3)
```

- Plot raw data

```
In [ ]:
```

- Save raw data

```
In [ ]: # if the data looks nice, save it!
```

### 3.3.2 Different bias currents

- Repeat 3.3.1 with another two bias currents and compare the three curves

The bias current was switched from  $I_b \approx ???\text{nA}$  to  $I_b \approx ???\text{nA}$ .

```
In [ ]: p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
    pyplane.Coach.BiasAddress.NTA_VB_N, \
    pyplane.Coach.BiasType.N, \
    pyplane.Coach.BiasGenMasterCurrent.I30nA, ???)])
```

```
In [ ]: # your codes
```

```
In [ ]: # plot the three curves on one figure to compare
```

**To conclude your observations:**

XXXXXXX

### 3.3.3 Different fixed voltages $V_n$

- Repeat 3.3.1 with another two fixed voltages  $V_2$  and compare the three curves

Switch voltage from  $V_2 = ???V$  to  $V_2 = ???V$ . The bias current was  $I_b = ???nA$

```
In [ ]: # Set V2 = ?
```

```
In [ ]: # Set Ib = ?
```

```
In [ ]: # your codes
```

```
In [ ]: # plot the three curves on one figure to compare
```

**To conclude your observations:**

xxx

## 3.4 Output current vs. input voltage

### 3.4.1 Basic measurement

- Set bias current  $I_b$

```
In [ ]: p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
    pyplane.Coach.BiasAddress.NTA_VB_N, \
    pyplane.Coach.BiasType.N, \
    pyplane.Coach.BiasGenMasterCurrent.I30nA, ???)])
```

Switch bias current back to  $I_b = ???nA$ .

- Assign common mode voltage  $V_{cm}$

```
In [ ]: Vcm_ex3 = ... # Vcm = ???V
```

- Sweep differential voltage  $V_{diff}$  and measure  $I_{out}$  (Hint: use `get_set_voltage` to get the real value set on the DAC)

```
In [ ]: import numpy as np
import time

V1_sweep_ex3 = np.arange(0.6, 1.2, 0.01) # voltage V1 sweep range

#V2_ex3_getset = p.get_set_voltage(pyplane.DacChannel.AIN4)

V2_ex3 = []
V1_sweep_ex3_getset = []
V2_ex3_getset = []
c2f_Iout_U0_Vcm_ex3 = []
c2f_Iout_UB0_Vcm_ex3 = []

for n in range(len(V1_sweep_ex3)):

    # calculate V2 via Vcm and V1
    V2_ex3.append(2*Vcm_ex3-V1_sweep_ex3[n])

    p.set_voltage(pyplane.DacChannel.AIN3,V1_sweep_ex3[n]) #
    p.set_voltage(pyplane.DacChannel.AIN4,V2_ex3[n]) #

    time.sleep(0.2) # settle time

    V1_sweep_ex3_getset.append(p.get_set_voltage(pyplane.DacChannel.AIN3))
    V2_ex3_getset.append(p.get_set_voltage(pyplane.DacChannel.AIN4))

    # read c2f values
    c2f_Iout_ex3_temp = p.read_c2f_output(0.1)
    c2f_Iout_U0_Vcm_ex3.append(c2f_Iout_ex3_temp[11])
    c2f_Iout_UB0_Vcm_ex3.append(c2f_Iout_ex3_temp[12])

# print(V1_sweep_ex3_getset)
# print(V2_ex3_getset)
# print(c2f_Iout_U0_Vcm_ex3)
# print(c2f_Iout_UB0_Vcm_ex3)
```

- Save raw data

```
In [ ]: # if the data looks nice, save it!
data_Iout_Vcm09_ex3 = [V1_sweep_ex3_getset,V2_ex3_getset,c2f_Iout_U0_Vcm_ex3,c2f_Iout_
# save to csv file
np.savetxt('./data/V1_sweep_Iout_Vcm09_ex3.csv', data_Iout_Vcm09_ex3, delimiter=',')
```

- Plot raw data (C2F frequency vs.  $V_{diff}$ )

```
In [ ]: import matplotlib.pyplot as plt
import numpy as np
plt.rcParams.update({'font.size': 15})
```

```

V1_sweep_Iout_Vcm09_ex3_getset,V2_Iout_Vcm09_ex3_getset,c2f_Iout_U0_Vcm09_ex3,c2f_Iout
Vdiff_Vcm09 = V1_sweep_Iout_Vcm09_ex3_getset-V2_Iout_Vcm09_ex3_getset
print(Vdiff_Vcm09)
c2f_Iout_Vcm09 = c2f_Iout_U0_Vcm09_ex3 - c2f_Iout_UB0_Vcm09_ex3
print(c2f_Iout_Vcm09)

plt.plot(Vdiff_Vcm09,c2f_Iout_Vcm09,'b+')

plt.xlabel('$V_1-V_2$ [V]')
plt.ylabel('C2F [Hz]')
plt.legend(['C2F'],prop={'size': 14})
plt.title('Fig. 12: Measured C2F data for $I_{out}$ plotted over $V_1-V_2$.')
plt.grid()
plt.show()


```

```

[-0.60000008 -0.58064526 -0.55953091 -0.53841656 -0.52082115 -0.49970675
-0.4785924 -0.4609971 -0.43988276 -0.41876841 -0.40117306 -0.38005871
-0.35894436 -0.34134907 -0.32023472 -0.29912025 -0.2815249 -0.26041055
-0.2392962 -0.22170091 -0.20058656 -0.17947215 -0.1583578 -0.14076245
-0.1196481 -0.09853375 -0.08093846 -0.05982405 -0.0387097 -0.02111435
0. 0.02111435 0.0387097 0.05982405 0.08093846 0.09853375
0.1196481 0.14076245 0.1583578 0.17947215 0.20058656 0.22170091
0.2392962 0.26041055 0.2815249 0.29912025 0.32023472 0.34134907
0.35894436 0.38005871 0.40117306 0.41876841 0.43988276 0.4609971
0.4785924 0.49970675 0.52082115 0.53841656 0.55953091 0.58064526]
[-5423. -5417. -5408. -5397. -5387. -5373. -5361. -5351. -5337. -5321.
-5303. -5283. -5256. -5228. -5199. -5157. -5116. -5053. -4982. -4903.
-4782. -4608. -4387. -4121. -3654. -2955. -2144. -784. 998. 2749.
3791. 4606. 5209. 5783. 6154. 6347. 6469. 6512. 6524. 6524.
6524. 6511. 6511. 6502. 6504. 6493. 6497. 6506. 6507. 6513.
6520. 6524. 6532. 6537. 6543. 6544. 6554. 6556. 6565. 6569.]

```

Fig. 12: Measured C2F data for  $I_{out}$  plotted over  $V_1 - V_2$ .

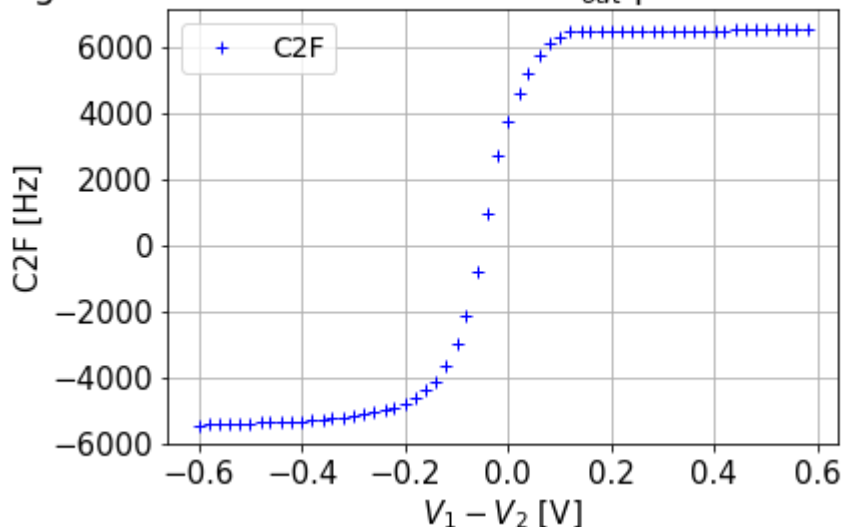

- Convert c2f frequency to current and plot. You may need the factors a2, a1, a0 that you get when fitting the  $I(f)$  function in section 3 to convert frequency to current.

In [ ]:

- Compute transconductance

In [ ]:

- Explain any asymmetries in the amplifier's I-V curve and the offset voltage in terms of mismatch between devices in the mirror and differential pair. Do you think we can distinguish the effects of mismatch in the current mirror and in the differential pair? The main point here is to recognize that there will be non-idealities, to understand where they arise.

### 3.4.2 Different bias currents

- Repeat 3.4.1 with another two bias currents and compare the three curves

In [ ]: `# Set Ib = ?`

The bias current was switched from  $I_b \approx ???\text{nA}$  to  $I_b \approx ???\text{nA}$ .

In [ ]:

**To conclude your observations:**

xxx

### 3.4.3 Different common mode voltages

- Repeat 3.4.1 with another two common mode voltages and compare the three curves

In [ ]: `# Assign common mode voltage Vcm  
Vcm_xxx = ???`In [ ]: `# Set Ib = ?`

The bias current was switched back to  $I_b \approx ???\text{nA}$ .

In [ ]: `# your code, data acquisition`

**To conclude your observations:**


xxxxxxx

**What do you observe when the common mode voltage  $V_{cm}$  is too small (e.g. 0.2V or 0.3V)? Does it have a sigmoid shape? If not, try to explain why.**

xxxxxx

# 4 P-Type 5T Transamp (OPTIONAL)

## 4.0 Schematic and pin map

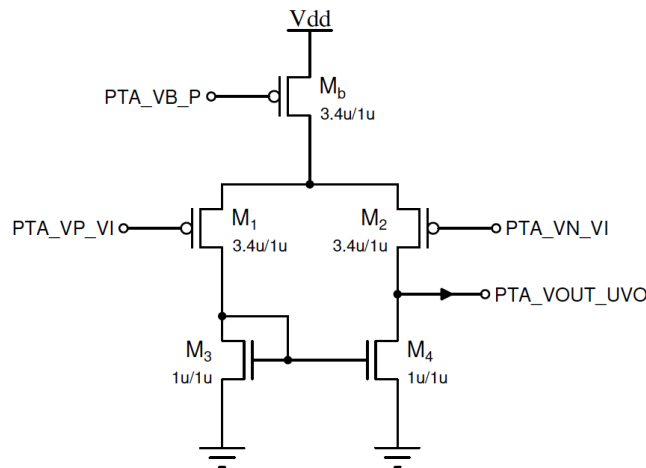

$$V_1 = V_p = \text{PTA\_VP\_VI} = \text{AIN7}$$

$$V_2 = V_n = \text{PTA\_VN\_VI} = \text{AIN8}$$

$$V_{out} = \text{PTA\_VOUT\_UVO} = \text{ADC}[12]$$

$$I_{out} = I_+ - I_- = \text{PTA\_IOUT\_UO} - \text{PTA\_IOUT\_UBO} = \text{C2F}[13] - \text{C2F}[14]$$

**Note:** There are three identical PTA circuits with the same bias and input voltages, one with the output open-circuited and routed out at PTA\_VOUTUVO, the other two with  $V_{out}$  fixed to 1V but  $I_{out}$  routed out through N- and P- type current mirror at PTA\_IOUT\_UO and PTA\_IOUT\_UBO.

## 4.1 Chip configuration

```
In [ ]: # configure P type TransAmp
p.send_coach_events([pyplane.Coach.generate_aerc_event( \
    pyplane.Coach.CurrentOutputSelect.SelectLine5, \
    pyplane.Coach.VoltageOutputSelect.SelectLine1, \
    pyplane.Coach.VoltageInputSelect.SelectLine1, \
    pyplane.Coach.SynapseSelect.NoneSelected, 0)])
```

## 4.2 Calibration of C2F channels

Here you need to calibrate PTA\_IOUT\_UO and PTA\_IOUT\_UBO in the same way as the last lab.

**Notice the W/L ratio of 3.4 of Mb.**

### 4.2.1 PTA\_IOUT\_UO



- Set fixed voltages for  $V_1$  and  $V_2$

```
In [ ]: p.set_voltage(pyplane.DacChannel.AIN7, ???) # V1 = ???
        p.set_voltage(pyplane.DacChannel.AIN8, ???) # V2 = ???
```

Set  $V_1 \gg V_2$ .

- Data acquisition (Hint: use master current 30 nA)

```
In [ ]: ...
        ...
        # Notice the W/L ratio of 3.4 of Mb when setting Ib.
        p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
            pyplane.Coach.BiasAddress.PTA_VB_P, \
            pyplane.Coach.BiasType.P, \
            pyplane.Coach.BiasGenMasterCurrent.I30nA, ???)])
        ...
```

- Plot

```
In [ ]:
```

- Save data

```
In [ ]: # if the data looks nice, save it!
```

- Extract the function  $I_+(f_+)$  (Hint: use higher order polynomial to increase accuracy)

```
In [ ]:
```

## 4.2.2 PTA\_IOUT\_UBO

- Set fixed voltages for  $V_1$  and  $V_2$

```
In [ ]: p.set_voltage(pyplane.DacChannel.AIN7, ???) # V1 = ??
        p.set_voltage(pyplane.DacChannel.AIN8, ???) # V2 = ??
```

Set  $V_1 \ll V_2$ .

- Data acquisition (Hint: use master current 30 nA)

```
In [ ]: # Notice the W/L ratio of 3.4 of Mb when setting Ib.
```

- Plot

In [ ]:

- Save data

In [ ]: *# if the data looks nice, save it!*

- Extract the function  $I_-(f_-)$  (Hint: use higher order polynomial to increase accuracy)

In [ ]:

## 4.3 Output voltage vs. input voltage

### 4.3.1 Basic measurement

- Set bias current  $I_b$

```
In [ ]: p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
    pyplane.Coach.BiasAddress.PTA_VB_P, \
    pyplane.Coach.BiasType.P, \
    pyplane.Coach.BiasGenMasterCurrent.I30nA, ???)])
```

The bias current is set to (Notice the W/L ratio of 3.4 of Mb.)

$$I_b = w \frac{BG_{\text{fine}}}{256} I_{BG_{\text{master}}} = 3.4 \frac{???}{256} \cdot 30\text{nA} = ???\text{nA}.$$

- Set fixed value of  $V_2$  (Hint: use get\_set\_voltage to get the real value set on the DAC)

```
In [ ]: p.set_voltage(pyplane.DacChannel.AIN8, ???) # V2 = ???
```

Set  $V_2 = ???\text{V}$ .

- Sweep  $V_1$  and measure  $V_{out}$  (Hint: use get\_set\_voltage to get the real value set on the DAC)

In [ ]:

- Plot raw data

In [ ]:

- Save raw data

```
In [ ]: # if the data looks nice, save it!
```

### 4.3.2 Different bias currents (optional)

- Repeat 4.3.1 with another two bias currents and compare the three curves

```
In [ ]:
```

Switch bias current from  $I_b = ???\text{nA}$  in the basic measurement to  $I_b = ???\text{nA}$ .

```
In [ ]:
```

**To conclude your observations:**

xxxxxxx

### 4.3.3 Different fixed voltages $V_n$ (optional)

- Repeat 4.3.1 with another two fixed voltages  $V_2$  and compare the three curves

```
In [ ]: p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
    pyplane.Coach.BiasAddress.PTA_VB_P, \
    pyplane.Coach.BiasType.P, \
    pyplane.Coach.BiasGenMasterCurrent.I30nA, ???)])
```

Switch bias current back to  $I_b = ???\text{nA}$ .

```
In [ ]: p.set_voltage(pyplane.DacChannel.AIN8, ???) # V2 = ???
```

- Repeat 4.3.1 with another two fixed voltages  $V_2$  and compare the three curves

```
In [ ]: p.set_voltage(pyplane.DacChannel.AIN8, ???) # V2 = ??
```

Switch input voltage from  $V_2 = ???\text{V}$  in the basic measurement to  $V_2 = \text{V}$ .

Switch bias current back to  $I_b = 7.5\text{nA}$ .

```
In [ ]: import numpy as np
import time

V1_sweep_ex4 = np.arange(0,1.8,0.05) # voltage V1 sweep range

V2_ex4_getset = p.get_set_voltage(pyplane.DacChannel.AIN8)

Vout_V1_sweep_ex4 = []
V1_sweep_ex4_getset = []

for n in range(len(V1_sweep_ex4)):
```

```

p.set_voltage(pyplane.DacChannel.AIN7,V1_sweep_ex4[n]) #

time.sleep(0.5) # settle time

V1_sweep_ex4_getset.append(p.get_set_voltage(pyplane.DacChannel.AIN7))
Vout_V1_sweep_ex4.append(p.read_adc_instantaneous(12))

print(V2_ex4_getset)
print(V1_sweep_ex4_getset)
print(Vout_V1_sweep_ex4)

```

In [ ]:

**To conclude your observations:**

xxxxxxx

## 4.4 Output current vs. input voltage

### 4.4.1 Basic measurement

- Set bias current  $I_b$

```

In [ ]: p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
    pyplane.Coach.BiasAddress.PTA_VB_P, \
    pyplane.Coach.BiasType.P, \
    pyplane.Coach.BiasGenMasterCurrent.I30nA, ???)])

```

Bias current is switched back to  $I_b = ???\text{nA}$ .

- Assign common mode voltage  $V_{cm}$

In [ ]: Vcm\_ex4 = ??

Common mode voltage is set to  $V_{cm} = ???\text{V}$ .

- Sweep differential voltage  $V_{diff}$  and measure  $I_{out}$  (Hint: use get\_set\_voltage to get the real value set on the DAC)

In [ ]:

- Plot raw data (C2F)

In [ ]:

- Save raw data

In [ ]: *# if the data looks nice, save it!*

- Convert rate to current and plot

In [ ]:

- Compute transconductance
- Explain any asymmetries in the amplifier's I-V curve and the offset voltage in terms of mismatch between devices in the mirror and differential pair, and the Early effect.

## 4.4.2 Different bias currents (optional)

- Repeat 4.4.1 with another two bias currents and compare the three curves

Switch bias current from  $I_b = ???\text{nA}$  in the basic measurement to  $I_b = ???\text{nA}$ .

In [ ]:

**To conclude your observations:**

xxxxxxx

## 4.4.3 Different common mode voltages (optional)

- Repeat 4.4.1 with another two common mode voltages and compare the three curves

The common mode voltage was changed from  $V_{cm} = ???\text{V}$  to  $V_{cm} = ???\text{V}$ .

In [ ]:

Switch bias current back to  $I_b = ???\text{nA}$ .


In [ ]:

**To conclude your observations:**

xxxxxxx

# 5 Wide-range Transamp

## 5.0 Schematic and pin map

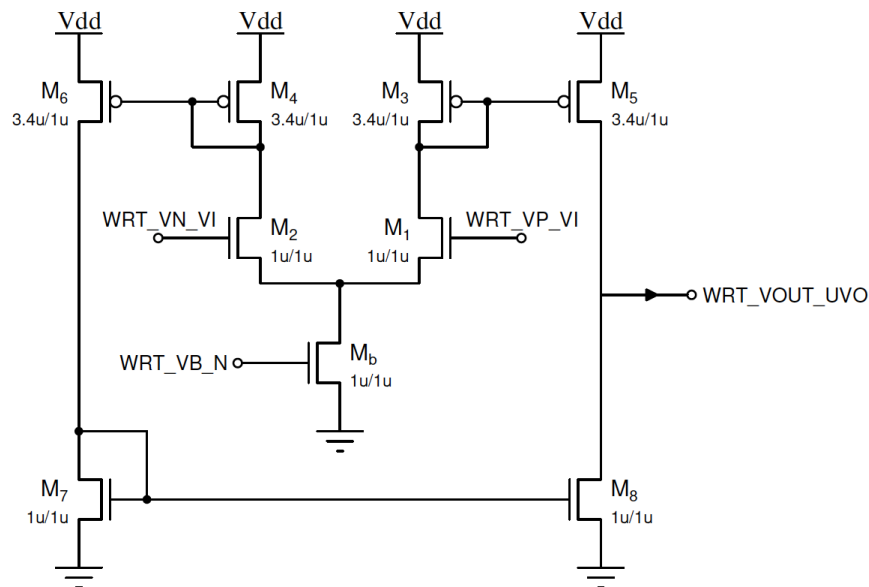

$$V_1 = V_p = \text{WRT\_VP\_VI} = \text{AIN7}$$

$$V_2 = V_n = \text{WRT\_VN\_VI} = \text{AIN8}$$

$$V_{out} = \text{WRT\_VOUT\_UVO} = \text{ADC}[11]$$

## 5.1 Chip configuration

```
In [ ]: # configure wide-range TransAmp
p.send_coach_events([pyplane.Coach.generate_aerc_event( \
    pyplane.Coach.CurrentOutputSelect.SelectLine5, \
    pyplane.Coach.VoltageOutputSelect.SelectLine1, \
    pyplane.Coach.VoltageInputSelect.SelectLine2, \
    pyplane.Coach.SynapseSelect.NoneSelected, 0)])
```

## 5.2 Output voltage vs. input voltage

### 5.2.1 Basic measurement

- Set bias current  $I_b$

```
In [ ]: p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
    pyplane.Coach.BiasAddress.WRT_VB_N, \
    pyplane.Coach.BiasType.N, \
    pyplane.Coach.BiasGenMasterCurrent.I30nA, 85)])
```

The bias current is set to

$$I_b = w \frac{BG_{\text{fine}}}{256} I_{BG_{\text{master}}} = \frac{85}{256} \cdot 30\text{nA} \approx 9.961\text{nA}.$$

- Set fixed value of  $V_2$  (Hint: use `get_set_voltage` to get the real value set on the DAC)

```
In [ ]: p.set_voltage(pyplane.DacChannel.AIN8,0.9) # V2 = 0.9
```

The input voltage is set to  $V_2 = 0.9\text{V}$ .

- Sweep  $V_1$  and measure  $V_{\text{out}}$  (Hint: use `get_set_voltage` to get the real value set on the DAC)

```
In [ ]: import numpy as np
import time

V1_sweep_ex5 = np.arange(0,1.8,0.05) # voltage V1 sweep range

V2_ex5_getset = p.get_set_voltage(pyplane.DacChannel.AIN8)

Vout_V1_sweep_ex5 = []
V1_sweep_ex5_getset = []

for n in range(len(V1_sweep_ex5)):

    p.set_voltage(pyplane.DacChannel.AIN7,V1_sweep_ex5[n]) #

    time.sleep(0.2) # settle time

    V1_sweep_ex5_getset.append(p.get_set_voltage(pyplane.DacChannel.AIN7))
    Vout_V1_sweep_ex5.append(p.read_voltage(pyplane.AdcChannel.AOUT11))

print(V2_ex5_getset)
print(V1_sweep_ex5_getset)
print(Vout_V1_sweep_ex5)
```

- Plot raw data

```
In [ ]:
```

- Save raw data

```
In [ ]: # if the data looks nice, save it!
```

## 5.2.2 Different bias currents

- Repeat 5.2.1 with another two bias currents and compare the three curves

The bias current is switched to  $I_b \approx ???\text{nA}$  from  $I_b \approx ???\text{nA}$  in the basic measurement.

```
In [ ]:
```

**To conclude your observations:**

XXXXXXXX

### 5.2.3 Different fixed voltages $V_n$

- Repeat 5.2.1 with another two fixed voltages  $V_2$  and compare the three curves

The bias current is switched back to  $I_b \approx ???\text{nA}$ .

```
In [ ]: # set Ib = ???
```

```
In [ ]: p.set_voltage(pyplane.DacChannel.AIN8, ???) # V2 = ???
```

```
In [ ]:
```

**To conclude your observations:**

XXXXXXXX

## 5.3 Comparison with 5T transamps

Compare the  $V_{out}$  vs  $V_{pos}$  ( $V_1$ ) curves of the three transamps with different  $V_{neg}$  ( $V_2$ )

```
In [ ]: # fix Vn = ??? (<0.9V), Compare Vout vs Vpos
```

```
# Read 5T NFET transamp
```

```
#Read wide-range transamp
```

```
In [ ]: #Read 5T PFET transamp
```

```
p.send_coach_events([pyplane.Coach.generate_biasgen_event(\
    pyplane.Coach.BiasAddress.PTA_VB_P, \
    pyplane.Coach.BiasType.P, \
    pyplane.Coach.BiasGenMasterCurrent.I30nA,25)])
```

```
p.set_voltage(pyplane.DacChannel.AIN8,1.1) #Set Vneg (V2)
```

```
V1_sweep_ex5 = np.arange(0,1.8,0.05) # voltage V1 sweep range
```

```
V2_ex5_getset = p.get_set_voltage(pyplane.DacChannel.AIN8)
```

```
Vout_V1_sweep_PFET = []
```

```
V1_sweep_ex5_getset = []
```

```
for n in range(len(V1_sweep_ex5)):
```

```
    p.set_voltage(pyplane.DacChannel.AIN7,V1_sweep_ex5[n]) #Set Vpos(V1)
```

```
    time.sleep(0.3) # settle time
```



```
V1_sweep_ex5_getset.append(p.get_set_voltage(pyplane.DacChannel.AIN7))
Vout_V1_sweep_PFET.append(p.read_voltage(pyplane.AdcChannel.AOUT12)) #Read Vout
```

```
In [ ]: # fix Vn = 0.9V, Compare Vout vs Vpos

plt.show()
```

```
In [ ]: #PFET configuration
p.send_coach_events([pyplane.Coach.generate_aerc_event( \
    pyplane.Coach.CurrentOutputSelect.SelectLine5, \
    pyplane.Coach.VoltageOutputSelect.SelectLine1, \
    pyplane.Coach.VoltageInputSelect.SelectLine1, \
    pyplane.Coach.SynapseSelect.NoneSelected, 0)])
```

```
In [ ]: # fix Vn = ??? (>0.9V), Compare Vout vs Vpos

plt.show()
```

**To conclude your observations:**

XXXXXXXX

## 6 Postlab

1. When we set the output voltage of the transconductance amplifier to a certain value between gnd and Vdd and measured its output current, we found that at some nonzero input voltage (the offset voltage) the output current was zero. Will we get a different input offset voltage if we change the output voltage? Explain why.

1. What are the conditions for keeping  $M_b$  in saturation for the P-type transamp? Do they differ from the N-type transamp?

1. What are the advantages and disadvantages of the wide-output-range transconductance amplifier vs. a standard transconductance amplifier? Consider layout area, output voltage swing, offset voltage, current asymmetries, and the gain A. Why is the wide-output-range transamp better suited for construction of a high-gain single-stage amplifier? *Hint: think about the necessary symmetries between pairs of transistors.*

## 7 What we expect after lab 4 and lab5

Can you sketch a transamp, a wide range transamp, a current correlator, and a bump circuit in

both n- and p-type varieties?

How does a differential pair work? How does the common-node voltage change with the input voltages? How can you compute the differential tail currents from the subthreshold equations, and how do you obtain the result in terms of the differential input voltage? How does a current-correlator work? How does a bump circuit work?

The I-V characteristics of a transconductance amplifier below threshold. What's the functional difference between simple and wide-output-range transamp? The subthreshold transconductance  $g_m$ . The relation between gain  $A$ , transistor drain conductances  $g_d$ , and transconductances  $g_m$ .

Can you reason through all the node voltages in these circuits? I.e., if we draw the circuit and provide specific power supply and input voltages, can you reason to estimate all the other node voltages, at least to first order approximations, assuming  $\kappa = 1$ ?

## 8 Congratulations

Wish you joy when you look back on your works, beautiful plots and all your efforts!